

M.Sc. 1st Semester Examination, 2024

ELECTRONICS

(Analog Electronics)

PAPER – ELC-104

Full Marks : 50

Time : 2 hours

Answer all questions

The figures in the right hand margin indicate marks

Candidates are required to give their answers in their own words as far as practicable

GROUP – A

Answer any four questions : 2×4


1. Define Q point.
2. Write two advantages of MOSFET.

3. What is thermal runaway ?
4. What is Miller effect ?
5. Write the concept of virtual ground of an OPAMP.
6. Write the advantages of an SMPS over linear regulated power supply.

GROUP – B

Answer any **four** questions : 4 × 4

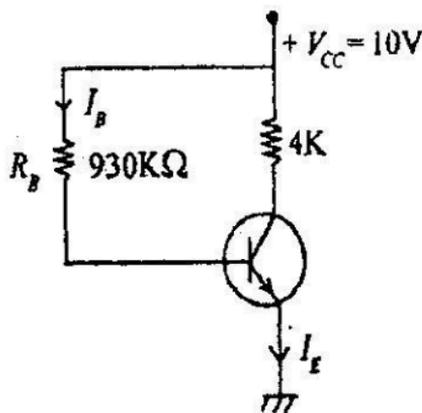7. Draw and explain positive clipper circuit. Give input and output waveform. $(1+2) + \left(\frac{1}{2} + \frac{1}{2}\right)$
8. Draw voltage transfer curve for BJT and indicate different operating regions. 2 + 2
9. A circuit is shown in figure below. It uses silicon transistor. Given that $\beta = 100$. Determine its operating point. 4



10. Draw and explain inverting comparator circuit using OPAMP with input and output waveforms. 2 + 2
11. Draw four feedback topologies used in electronic circuits. 1 + 1 + 1 + 1
12. Draw three configurations of MOSFET. Draw PI model of a MOSFET. 3 + 1

GROUP – C

Answer any **two** questions : 8 × 2

13. Draw small signal equivalent circuit of a


common emitter amplifier. Derive voltage gain, input impedance and output impedance of the circuit.

2 + 2 + 2 + 2

14. Draw and explain instrumentation amplifier using three OPAMP configurations. 2 + 6

15. Write down channel length modulation phenomenon of MOSFET. For the circuit shown in below, find the value of R that results in $V_D = 0.8$ V. The MOSFET has $V_{th} = 0.5$ Volt. $\mu_n C_{ox} = 0.4$ mA/V², $W/L = 0.72$ μ m/0.18 μ m, $\lambda = 0$.

4 + 4

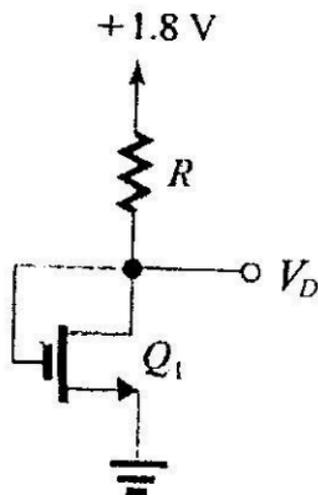

16. Draw and explain triangular wave generator circuit. Give input and output waveforms.

(2 + 4) + (1 + 1)

[Internal Assessment – 10 Marks]
