

**M. Sc. 1st Semester Examination, 2024****ELECTRONICS***(Analog Circuit Design Lab)**( Practical )*

PAPER – ELC-196

*Full Marks : 50**Time : 3 hours*Answer **all** questions*The figures in the right hand margin indicate marks*

Perform any **one** of the following experiment selecting by a draw :

1. Design a R-C phase shift oscillator of frequency \_\_\_\_\_ (to be supplied during examination). Implement the circuit and compare design and theoretical value.

2. Design an integrator circuit using OPAMP. Implement the circuit and find the transfer characteristics.
3. Design a first order active low pass filter with cut-off frequency \_\_\_\_\_ (to be supplied during examination). Implement the circuit and find cut-off frequency.
4. Design a first order active high pass filter with cut-off frequency \_\_\_\_\_ (to be supplied during examination). Implement the circuit and find cut-off frequency.
5. Design a second order active low pass filter with cut-off frequency \_\_\_\_\_ (to be supplied during examination). Implement the circuit and find cut-off frequency.
6. Design a second order active high pass filter with cut-off frequency \_\_\_\_\_ (to be supplied during examination). Implement the circuit and find cut-off frequency.

7. Design and implement a regulated power supply using LM 317. Find load and line regulation.
8. Design a fixed biased transistor circuit. Find  $I_C$ ,  $I_B$ ,  $I_E$ ,  $V_{BE}$ ,  $V_{CE}$ ,  $V_{CB}$ . Draw the load line. Study the change of load line with change in  $V_{CC}$ .
9. Design a self bias transistor circuit with  $R_E$ . Study the change in  $I_C$  with variation of  $\beta$  of transistor. Study the frequency response.
10. Design a self bias transistor circuit with  $R_E$ . Study the change in  $I_C$  with variation of  $\beta$  of transistor. Study the frequency response.
11. Design and implement a regulated power supply of \_\_\_\_\_ volt and \_\_\_\_\_ mA current (to be supplied during examination). Find load and line regulation.

12. Design a differentiator circuit using OPAMP. Implement the circuit and find the transfer characteristics.

### Marks Distribution

Circuit design	– 15 Marks
Implementation	– 10 Marks
Record of data	– 10 Marks
Viva-voce	– 10 Marks
Laboratory Note Book	– 05 Marks
<hr/>	
Total :	– 50 Marks