

M.Sc. 1st Semester Examination, 2024

PHYSICS

(Digital Electronics)

PAPER—PHS-108

Full Marks : 25

Time : 1 hour

Answer all questions

The figures in the right hand margin indicate marks

Candidates are required to give their answers in their own words as far as practicable

GROUP — A

Answer any two questions : 2×2


- 1. In a 4-bit asynchronous counter every flip-flop has 100 nsec propagation delay. Determine the maximum frequency of the clock pulse that can be used in that counter.**

(Turn Over)

2. Give the equivalent digital circuit of the following Karnaugh map :

AB \ CD	00	01	11	10
00	1			1
01		1	1	
11		1	1	
10	1			1

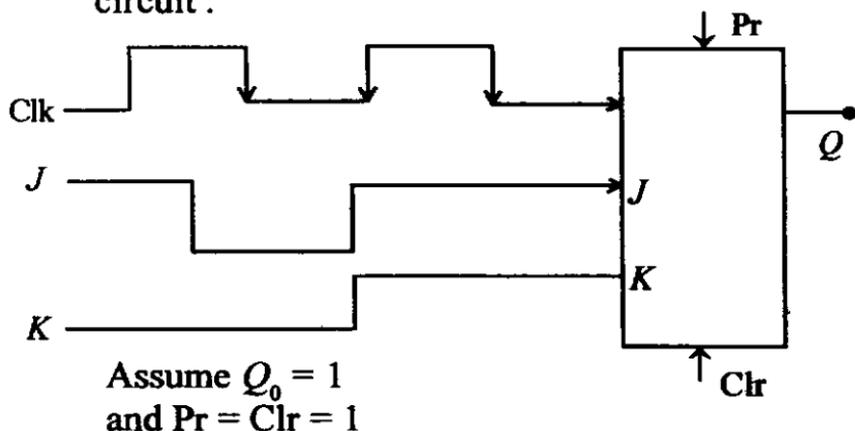3. Give the output waveform for the following circuit :




4. What do you mean by astable, monostable and bistable multivibrator ?


GROUP – B

Answer any two questions : 4×2

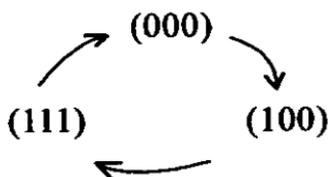5. Design a circuit which has the following state diagram :



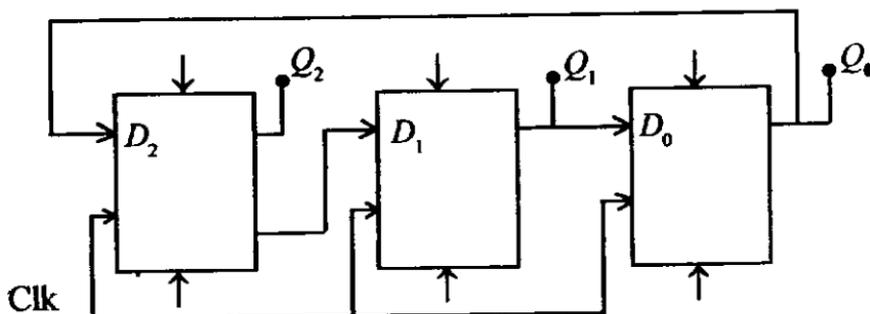6. Write down the different output states of the following Flip flop circuit. Explain the operation assuming the initial output as (000).



7. What do you mean by universal register ?
Draw the circuit of 3-bit PISO register. 1 + 3
8. (a) In a 4-bit digital circuit the input is in BCD form and output goes high when the input is equivalent to a prime number. Write down the truth table.
- (b) Draw a circuit to check two digital signals, $A(A_1 A_0)$ and $B(B_1 B_0)$, are equal or not. 2 + 2

GROUP – C

Answer any **one** question : 8 × 1

9. (a) Draw a circuit of 3-bit synchronous up/down counter with a mode selector for selecting upcount or down count.
- (b) Design a circuit which can convert a 10 KHz signal into 1 KHz signal and explain its operation. 4 + 4

10. (a) Convert a JK FF into a T FF.

(b) Draw the circuit of 3-bit bi-directional SISO register which can flow data from left to right or right to left in a controlled way.

4 + 4

[Internal Assessment — 5 Marks]

